

PCB Power Distribution Board

Team I : Lunar ROADSTER

Ankit Aggarwal, Deepam Ameria, Bhaswanth Ayapilla, Simson D'Souza, Boxiang Fu

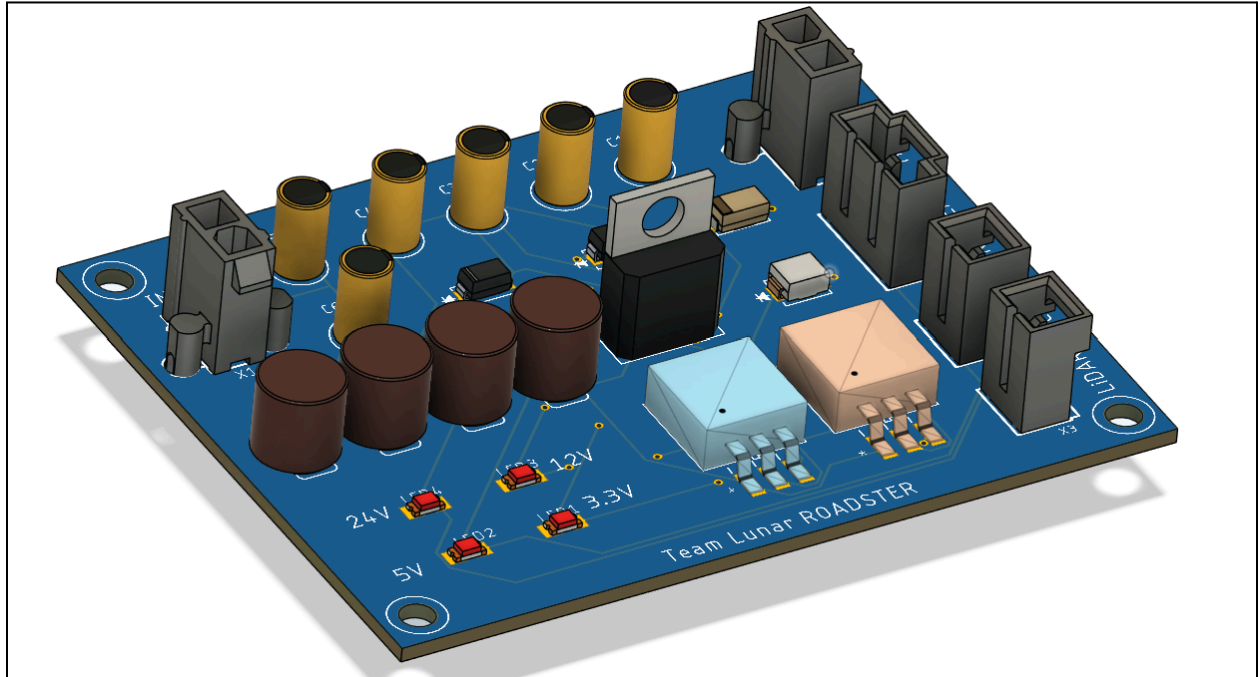


Figure 1: Isometric View of the Power Distribution Board PCB

Section 1: Design

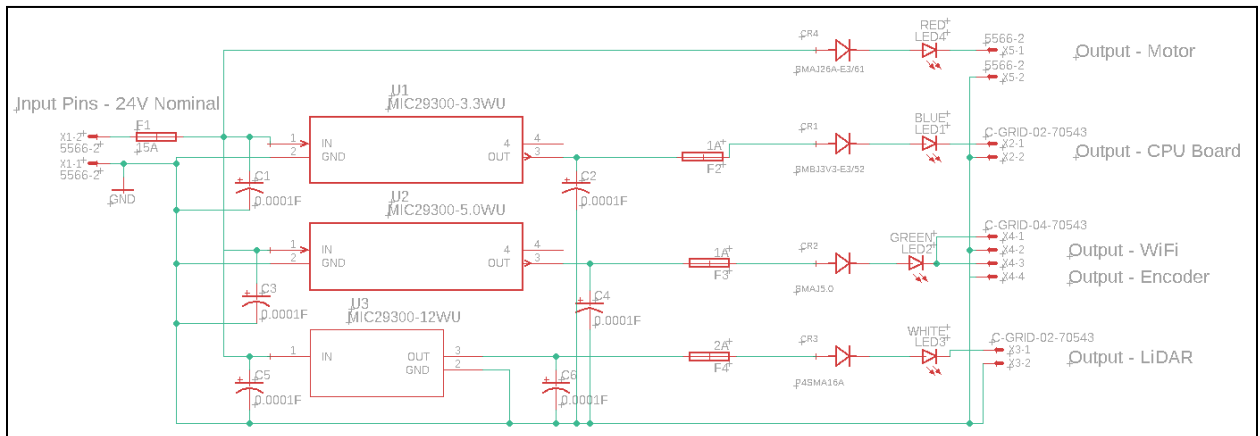


Figure 2: Schematic of the Power Distribution Board PCB

Bill of Materials

| Part | Value | Device | Package | Description |
|------|-------------------|-------------------|---------------------|---|
| C1 | 0.0001F | CPOL-USE2. 5-6 | E2,5-6 | POLARIZED CAPACITOR, American symbol |
| C2 | 0.0001F | CPOL-USE2. 5-6 | E2,5-6 | POLARIZED CAPACITOR, American symbol |
| C3 | 0.0001F | CPOL-USE2. 5-6 | E2,5-6 | POLARIZED CAPACITOR, American symbol |
| C4 | 0.0001F | CPOL-USE2. 5-6 | E2,5-6 | POLARIZED CAPACITOR, American symbol |
| C5 | 0.0001F | CPOL-USE2. 5-6 | E2,5-6 | POLARIZED CAPACITOR, American symbol |
| C6 | 0.0001F | CPOL-USE2. 5-6 | E2,5-6 | POLARIZED CAPACITOR, American symbol |
| CR1 | SMBJ3V3-E3 /52 | SMBJ3V3-E3 /52 | CR_V3-E3/52_V IS | Diode |
| CR2 | SMAJ5.0 | SMAJ5.0 | SMASERIES_LT F | Diode |
| CR3 | P4SMA16A | P4SMA16A | P4SMASERIES_ LTF | Diode |
| CR4 | SMAJ26A-E3 /61 | SMAJ26A-E3 /61 | DIODE_DO-214 AC | Diode |
| F1 | 15A | TE5 | TE5 | FUSE |
| F2 | 1A | TE5 | TE5 | FUSE |
| F3 | 1A | TE5 | TE5 | FUSE |
| F4 | 2A | TE5 | TE5 | FUSE |
| LED1 | BLUE | LEDSMT120 6 | 1206 | LED |
| LED2 | GREEN | LEDSMT120 6 | 1206 | LED |

| | | | | |
|------|-----------------|-----------------|--------------------|--------------------------|
| LED3 | WHITE | LEDSMT1206 | 1206 | LED |
| LED4 | RED | LEDSMT1206 | 1206 | LED |
| U1 | MIC29300-3.3WU | MIC29300-3.3WU | TO-263-3_MCL | Voltage Regulator |
| U2 | MIC29300-5.0WU | MIC29300-5.0WU | TO-263-3_MCL | Voltage Regulator |
| U3 | MIC29300-12WU | MIC29300-12WU | TO220-3LD-PL-1_MCH | Voltage Regulator |
| X1 | 5566-2 | 5566-2 | 5566-2 | Mini FIT connector 2 pol |
| X2 | C-GRID-02-70543 | C-GRID-02-70543 | 70543-02 | CONNECTOR |
| X3 | C-GRID-02-70543 | C-GRID-02-70543 | 70543-02 | CONNECTOR |
| X4 | C-GRID-04-70543 | C-GRID-04-70543 | 70543-04 | CONNECTOR |
| X5 | 5566-2 | 5566-2 | 5566-2 | Mini FIT connector 2 pol |

Section 2: Layout

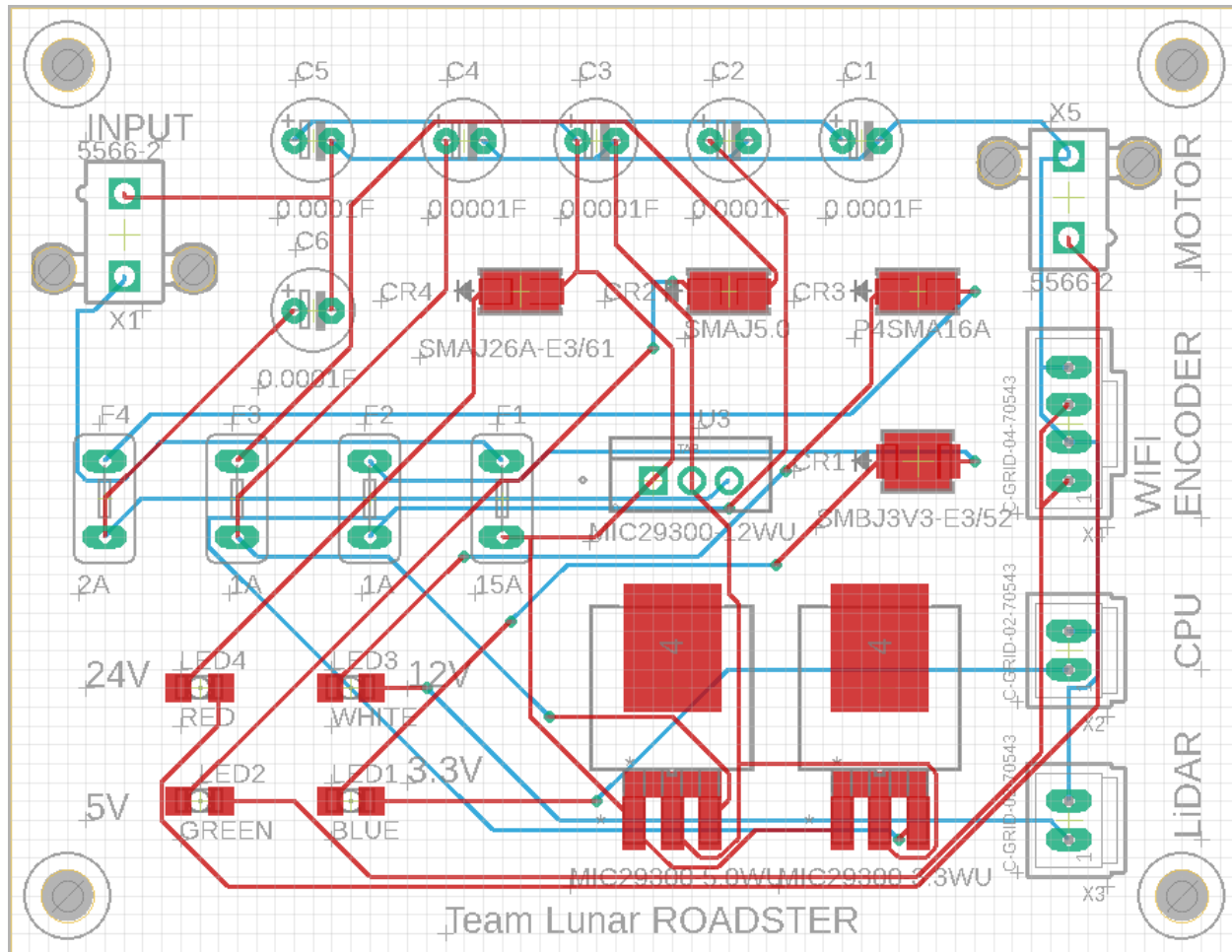


Figure 3: Board Layout of the Power Distribution Board PCB

Section 3: Analysis and Documentation

1. Linear Regulators:

The efficiency of each regulator is:

>> MIC29300-3.3WU: $1 - ((24 - 3.3) / 24) = 1 - 0.8625 = 0.138 = 13.8\%$

>> MIC29300-5.0WU: $1 - ((24 - 5) / 24) = 1 - 0.792 = 0.208 = 20.8\%$

>> MIC29300-12WU: $1 - ((24 - 12) / 24) = 1 - 0.5 = 0.5 = 50\%$

2. Subsystems:

The input power used by each subsystem is:

a) CPU board: $P = 3.3 \text{ W}$

b) Wifi and Encoder: $P = 5 \text{ W}$

c) LIDAR: $P = 24 \text{ W}$


d) Motor: $P = 240 \text{ W}$

3. Total System Efficiency

= Max. Output Power / Max. Input Power

$$= (3.3 + 5 + 24 + 240) / (24 \times 14) = 272.3/336 = 81.04\%$$

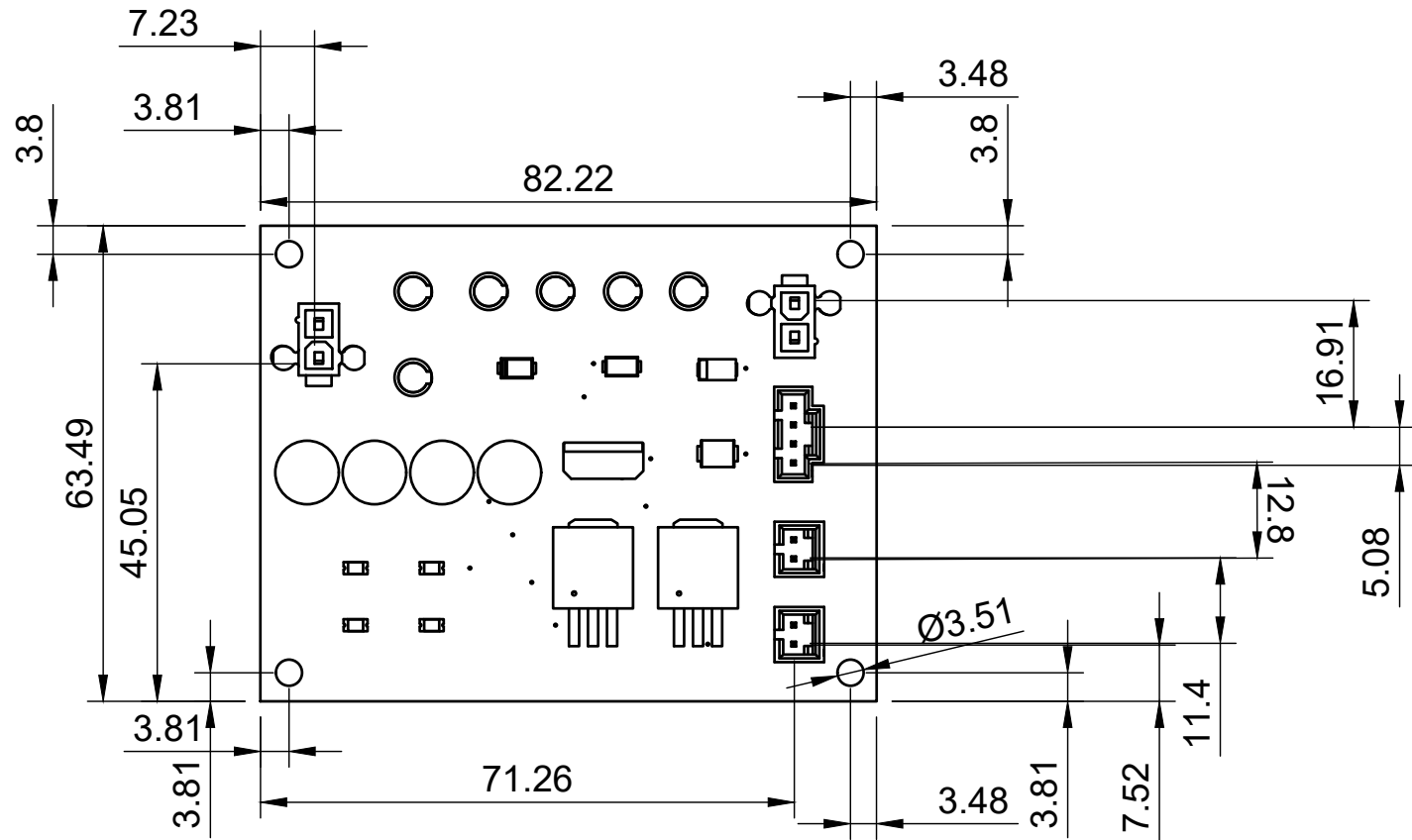Mechanical Drawing is attached after this document.



Scale - 1:1

All dimensions are in mm
All connectors are
dimensioned based on PIN1.

| | | | | | |
|-------------|---------------------|--|------------------------------------|-----------------------------|--------------|
| Dept. RI | Technical reference | Created by Ankit Aggarwal 14-02-2025 | Approved by Team Lunar ROADSTER | | |
| | | Document type Mechanical Drawing | Document status Finalized | | |
| | | Title PCB Assembly Power Distribution Board | DWG No. | | |
| | | | Rev. 1.0 | Date of issue 02/01/2024 | Sheet 1/1 |